

Hall Ticket No.:

--	--	--	--	--	--	--	--	--	--

Set-1

Course Code: 23MTVLT01

MALINENI LAKSHMAIAH WOMEN'S ENGINEERING COLLEGE
(AUTONOMOUS)

I - M.Tech. I - Semester (MR23) Regular Examinations, March - 2024


CMOS ANALOG IC DESIGN**Department of Electronics & Communication Engineering**


Time: 3 hours

Max. Marks: 75

Answer **ALL** the questions – 5*15=75 Marks

Q. No.	Question	Marks	CO	BL
1	a) Explain about Short channel Effects for MOS Transistor.	(7M)	CO1	L3
	b) Derive the expression for I/V Characteristics of MOS Transistor and obtain the relationship between I_D of MOSFET and its terminal voltage.	(8M)	CO1	L4
(OR)				
2	a) Using small signal analysis, Derive an expression for the output resistance of the cascode current source.	(8M)	CO1	L3
	b) With necessary schematics, obtain the small-signal model of CS stage including transistor output resistance.	(7M)	CO1	L4
3	a) Explain why the Gilbert cell can operate as an analog voltage multiplier.	(8M)	CO2	L3
	b) Sketch the Input-Output characteristics of a differential pair and explain its operation.	(7M)	CO2	L4
(OR)				
4	a) With relevant expression of active current mirror signal of the differential pair with current-source load and calculate the value of g_m and R_{out}	(8M)	CO2	L3
	b) Discuss about the Common-mode properties of the differential pair with active current mirror	(7M)	CO2	L3
5	a) Explain about the high frequency model of common-source stage and sketch the characteristics	(7M)	CO3	L4
	b) For the common-gate stage shown in Fig(a), calculate the transfer function and the input impedance, Z_{in} . Explain why Z_{in} becomes independent of C_L as the capacitance increases	(8M)	CO3	L4

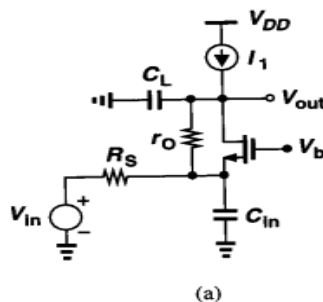

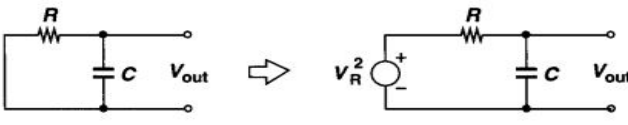(OR)					
6	a	Explain about the different types of Noises generated in Integrated Circuits	(8M)	CO3	L4
	b	Consider the RC circuit shown in fig (b), calculate the noise spectrum and the total noise power in V_{out} 	(7M)	CO3	L3

7	a	Discuss briefly about the different Feedback topologies with necessary Schematics	(15M)	CO4	L3
(OR)					
8	a	Explain about Two-stage opamp with single-ended output with neat sketch	(7M)	CO4	L3
	b	State and discuss about the Slew rate in the linear op amp circuit	(8M)	CO4	L3

9	a	what is a comparator and list the important characteristics of a comparator	(8M)	CO5	L4
	b	Explain about Open loop comparator	(7M)	CO5	L4
(OR)					
10	a	With relevant schematics explain about discrete-time comparators.	(8M)	CO5	L3
	b	How to improve the performance of an open loop high gain comparator by auto zeroing?	(7M)	CO5	L3
